

# Wireless Resonant Converter Engineering Review


Zachary Hoffman  
Department of Electrical Engineering  
*January 2024*

# About Me

- Electrical Engineering BS and MS
- Research assistant in Oceans  
Department of Doerr School of  
Sustainability
- 2 year captain of Men's Lacrosse
- Photography
- Love the outdoors!
- 49ers fan and dog named Kobe




# Presentation Overview

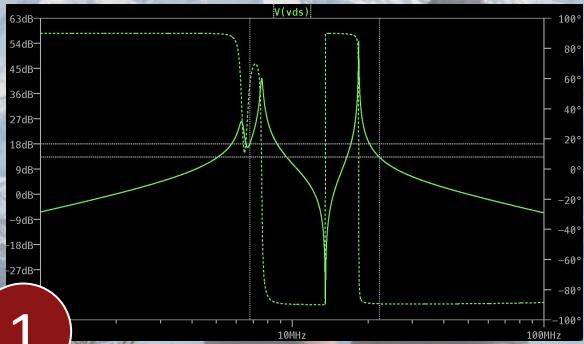

1
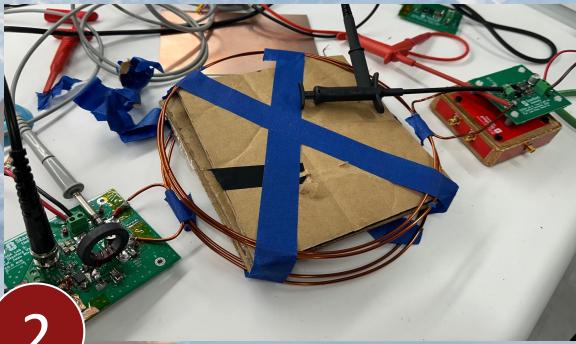
## Inverter Specification and Design


- Project Requirements
- Resonant converter Overview
- Design and Strategy



2
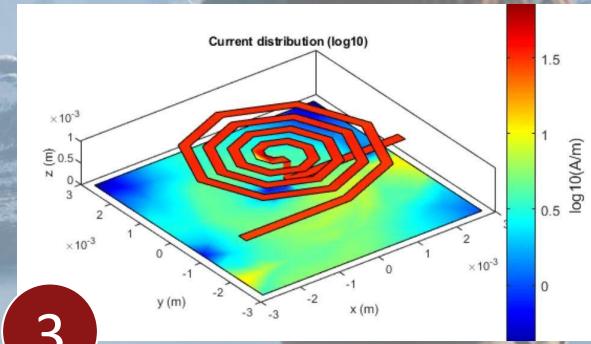
## Inverter Implementation, Testing, and Results

- Inverter
- Transformer Coil
- Testing and Results



3

## Manufacturing and Next Steps (lessons from De-Ice)

- Reviewing main manufacturing issues
- Manufacturing Magnetics

A photograph of a person's hands reaching up towards a large, layered rock formation. The hands are positioned as if trying to touch or climb the rock. The rock face is composed of numerous horizontal layers of sedimentary rock, showing various shades of brown, tan, and reddish-brown. A person's arm and shoulder are visible on the right side of the frame, wearing a dark long-sleeved shirt and a black digital wristwatch. In the top left corner, there is a red circular graphic containing the number '1'.

1

# Inverter Specification and Design

# 1 Converter Requirements

## EE356 Final Project Deliverables

1. Deliver 25 W of DC power
2. Operate at **6.78 MHz**
3. Utilize a minimum input of 20V
4. Transmit power wirelessly (>1 in)



[https://www.adafruit.com/product/2162?gclid=CjwKCAiA75itBhA6EiwAkho9e7AIgQgyucyarSMNLOlmpIHTVSmdQLQafFawWS8Zif4hR8g2ISXLUUxoCBj0QAvD\\_BwE](https://www.adafruit.com/product/2162?gclid=CjwKCAiA75itBhA6EiwAkho9e7AIgQgyucyarSMNLOlmpIHTVSmdQLQafFawWS8Zif4hR8g2ISXLUUxoCBj0QAvD_BwE)

# 1 Converter Requirements

Why would you want this?

- School design challenge for learning purposes
- Requirements aren't necessarily motivated by real life
- **High frequency** wireless converters may have benefits for certain applications
- Is emblematic of power electronic problems with real world applications



<https://evchargingsummit.com/blog/everything-you-need-to-know-about-wireless-ev-charging/>

# 1 Resonant Converter Review

## Characteristics of DC-DC


- Switch network
- **Resonant tank**
- Rectifier

## Advantages of Resonant Converter


- Lump parasitics into design
- Diminish switching losses (**ZVS or ZCS**)
- Ability to easily generate high voltage, high frequency sinusoidal outputs

## Common uses

- Ballasts for gas-discharge lamps
- Broadcasting
- Ionizing gas for IC plasma etching

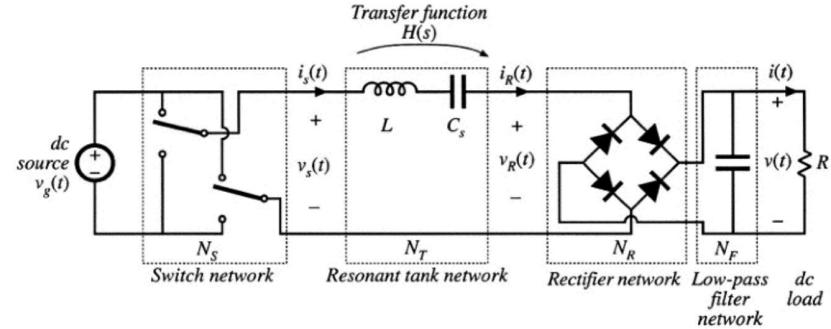

pg 707

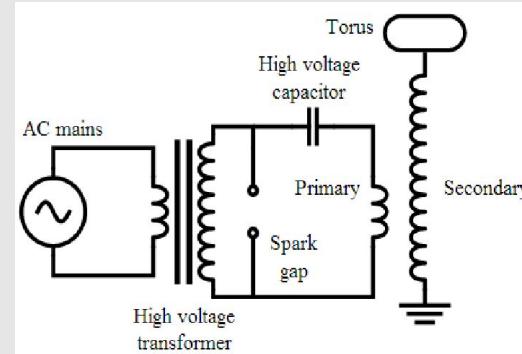

[https://www.researchgate.net/figure/Tesla-coil-circuit-diagram-5\\_fig5\\_283186438](https://www.researchgate.net/figure/Tesla-coil-circuit-diagram-5_fig5_283186438)


# 1 Design Strategy

## Class E Amplifier

- Resonance set with **LCC topology**
- Lump in drain capacitance
- ZVS
- One switch!
- Large input filter
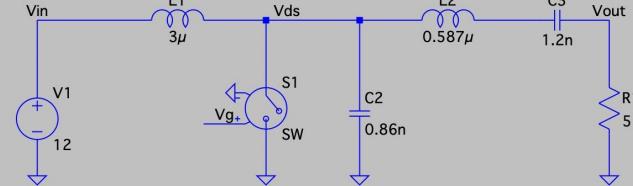
### Class E Amplifier

$Q_{LL} = 5$   
 $L_s = 0.587 \mu\text{H}$   
 $C_{LP} = 0.862 \text{nF}$   
 $C_{LS} = 1.2 \text{nF}$   
 $L_{\text{choke}} = 3 \mu\text{H}$




.tran {T/150} 10m {10m - T \* 3} {T/150} UIC

.param D = 0.5  
.param f = 6.78Meg  
.param T = {1/f}

Vg  
PULSE(-1 0 1n 1n {D\*T} {T})

.model SW SW(Ron=1u Roff=1MEG)

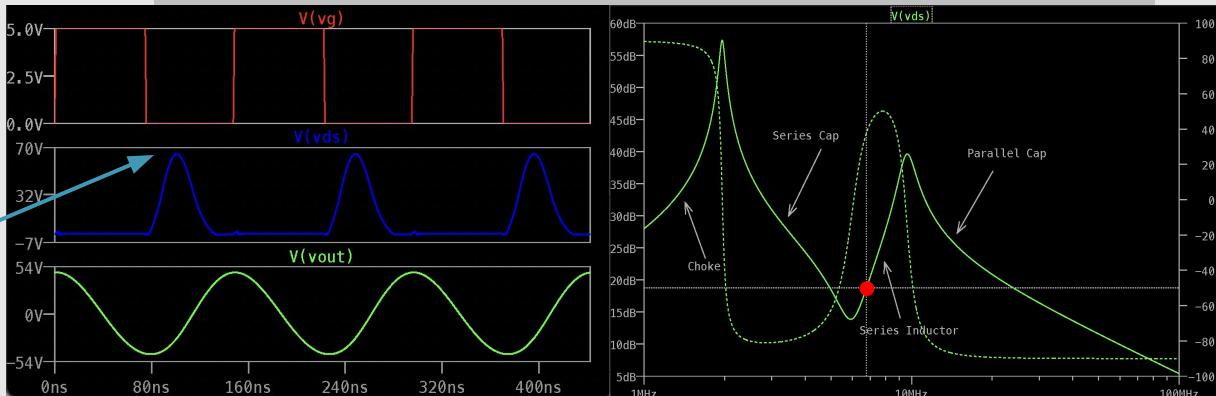



## Drawbacks

- Currently tuned to 5 ohm
- Large drain voltage
- $V_{d\max} = 4 \times V_i$

# 1 Design Strategy
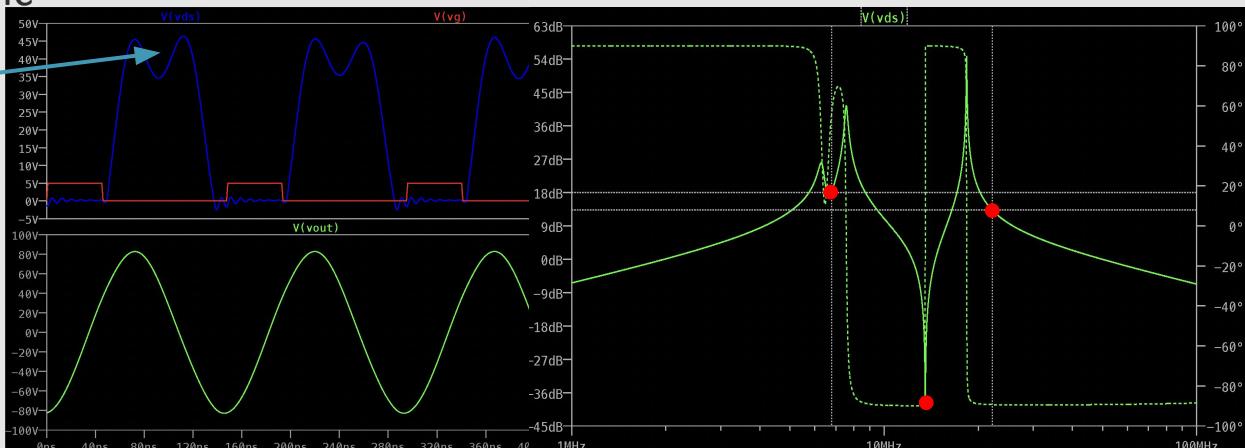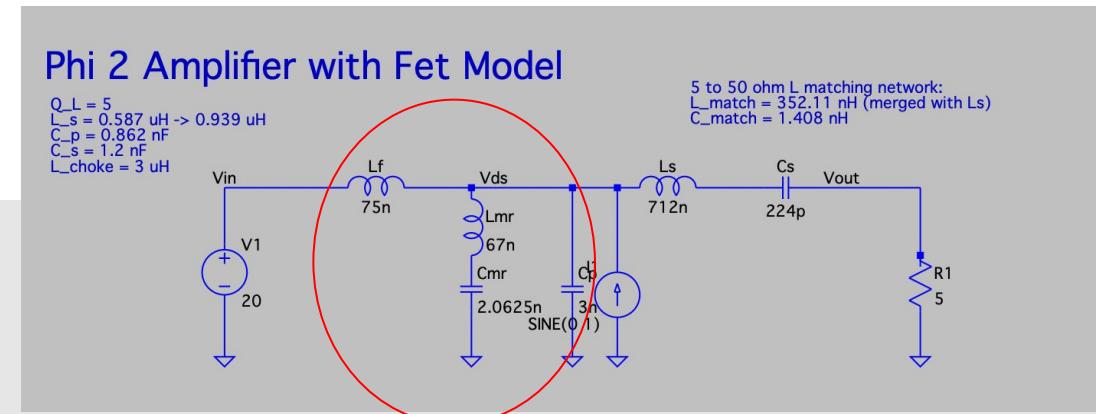
## $\Phi_2$ Inverter

- Added “input filter”
- Eliminate second harmonic
- Still ZVS
- $V_{d\max} = 2 \times V_i$




## Drawbacks

- Still tuned to 5 ohm
- More magnetics!
- More resonant points!
- High transient currents in filter
- Poorer input filter

# 1 Design Strategy
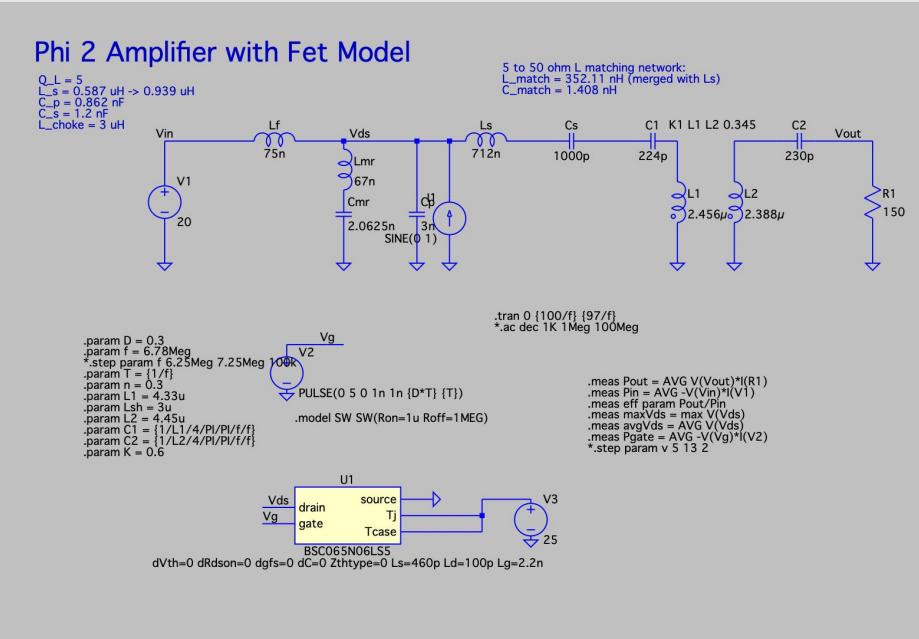
# Addressing Wireless, DC, and Power Requirements

- Design a **wireless transformer**
  - Address impedance of transformer and rectifier
  - Keep in mind high frequency considerations such as skin effect, proximity effect, radiation losses, etc.
  - Choose load that can be achieved experimentally



2

# Inverter Implementation, Testing, and Results





## 2

# Wireless Coil Design
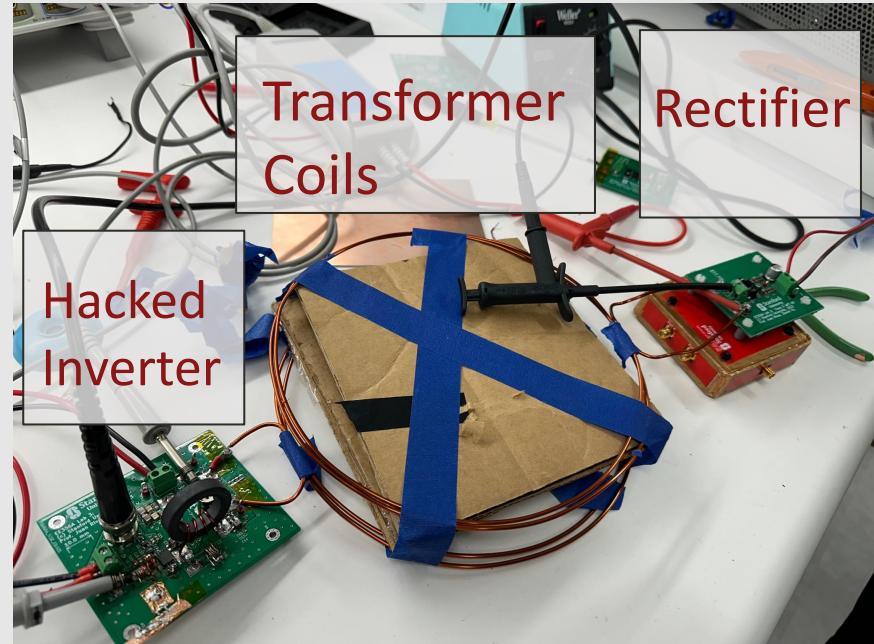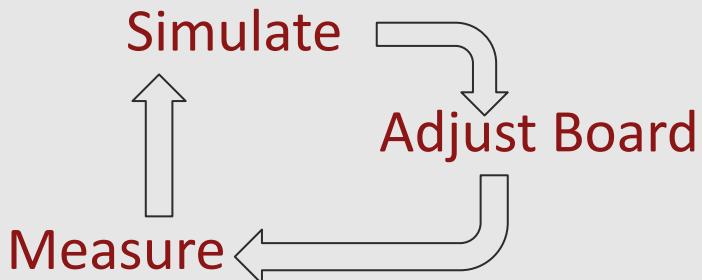
## Components and Design Steps

- “Hacked” Class E Amplifier
- Characterized wireless coils with VNA
- Characterize drain impedance with VNA and compare with simulation
- Attach Rectifier and deal with non linearities
- TUNE!



## 2


# Our Wireless Transformer Implementation

Three main challenges


1. Avoiding **self resonance**
2. Achieving strong coupling between two coils
3. Dealing with large reactance

Ways to address challenges

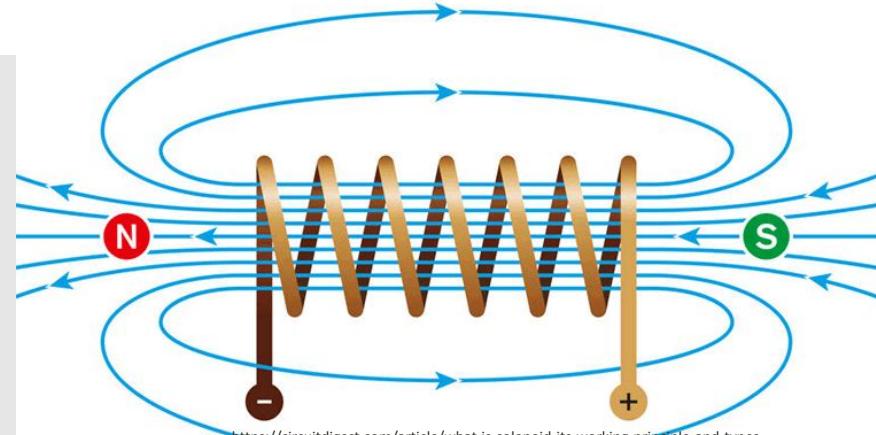1. Reduce number of turns
  - a. But  $B = \mu NI/L$
2.  $\Phi=BA$
3. Cancel with series capacitors


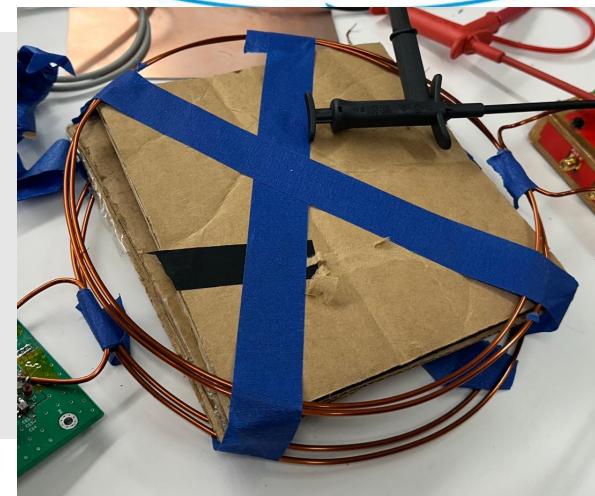
<https://circuitdigest.com/article/what-is-solenoid-its-working-principle-and-types>




# 2 Testing and Results

## Testing

- The discontinuities of the rectifier created a lot of issues
- Blew up a number of FETs (when not ZVS)
- Used power attenuator and tuned to 50 ohms
- Shifting frequency showed we were not perfectly tuned
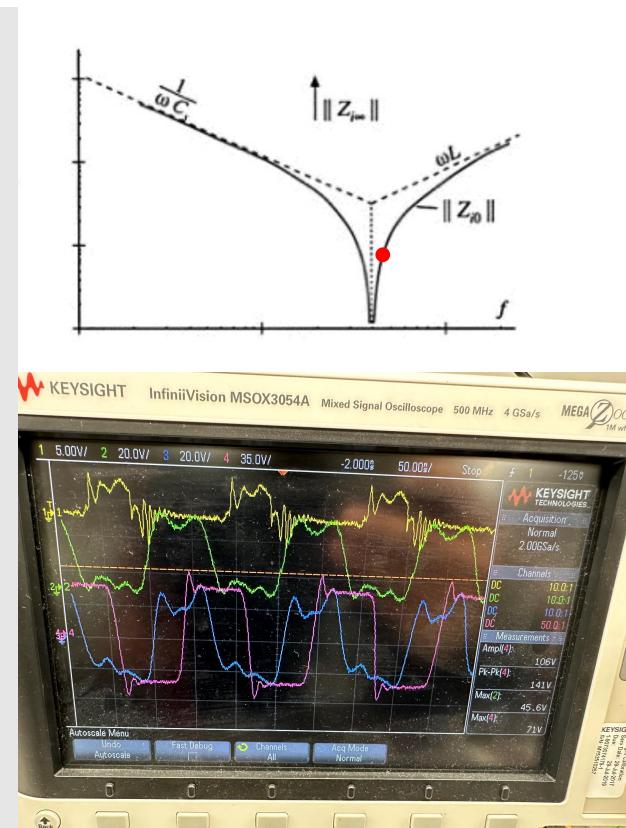
## Results

- Achieved required goals
- Characterized **frequency, load, Vin**





3

# Manufacturing and Next Steps (Lessons from DeIce)

## 3

# Manufacturing Considerations

Major challenges (to name a few)

EMI      Reliability      Durability      Cost



MAGNETICS



Getting rid of airplane  
de-icing delays **for good.**




## 3

# Planar Trace Inductors
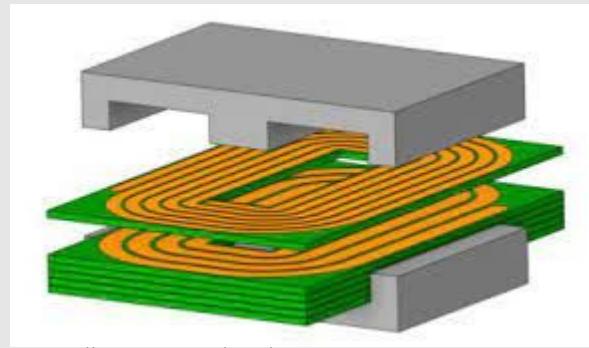
## Ferrite Core Cutouts


- Can achieve higher inductances ✓
- Experience saturation ✗
- Higher core losses ✗
- Fragile and take up space ✗



<https://ieeexplore.ieee.org/stamp/stamp.jsp?arnumber=10210576>
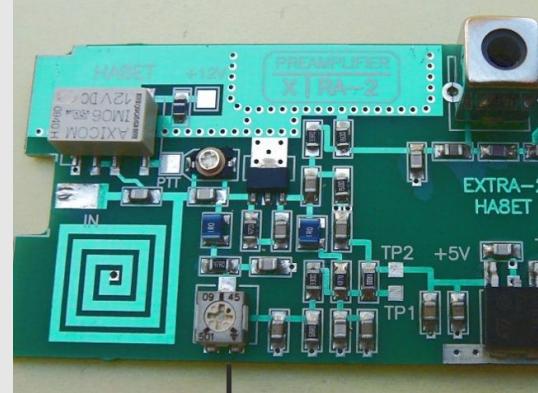
## Spiral Inductors

- Air core
  - low losses, no saturation ✓
- Space efficient ✓
- Easier heat management ✓
- Lower inductances (harder to model) ✗
- Higher conduction losses ✗




<https://coil32.net/pcb-coil.htm>

# 3

# Planar Trace Inductors

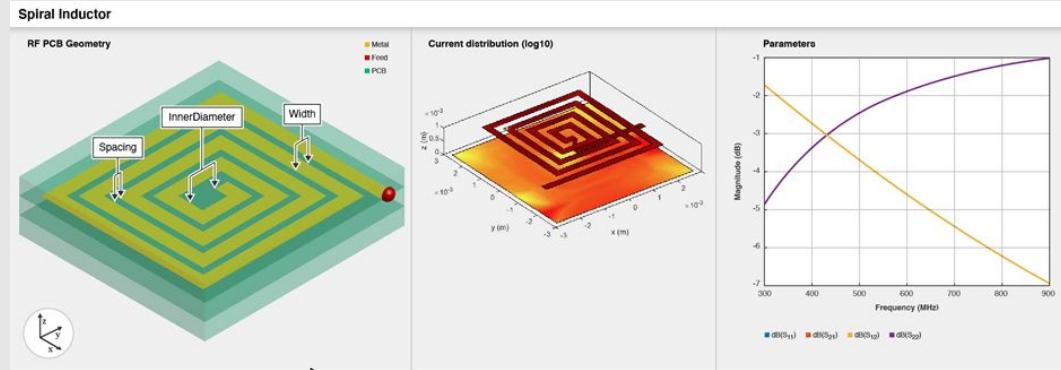
## Considerations

- Geometry
  - Number of turns and shape
- Number of Layers
- Power requirements
- Power dissipation ability


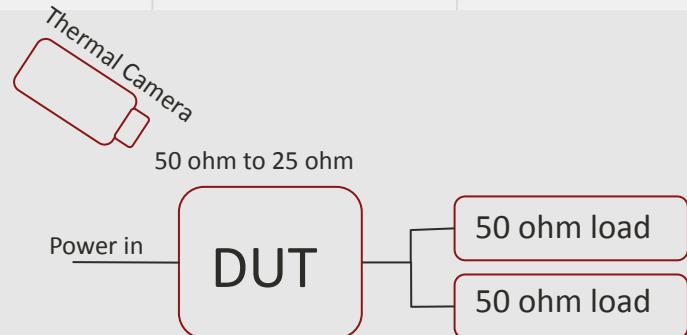
## Strategy

- Work with mechanical team to discuss geometric requirements and heat sink
- Simulate using finite element software
  - Use S parameters to estimate power losses
- Spin coupon boards
- Characterize and power test



# 3


# Findings and Manufacturing Recommendations

## Findings


- Robust thermal interface necessary for power
- Modulating ground plane distance proved best method for tuning
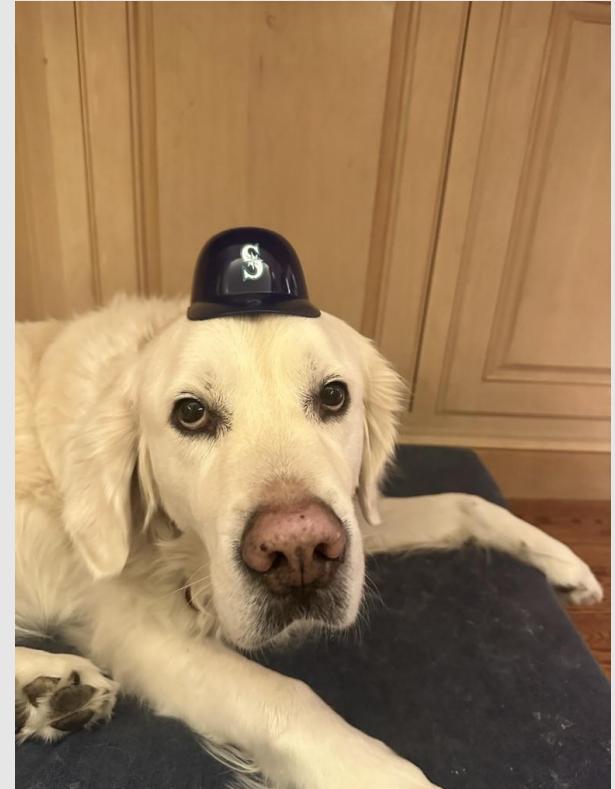
## Manufacturing Recommendations

- Catalog handful of inductor CAD designs
- Use washers for spacing and tuning
- Ground plane should also serve as heat sink
- Use lots of vias!




# Presentation Overview

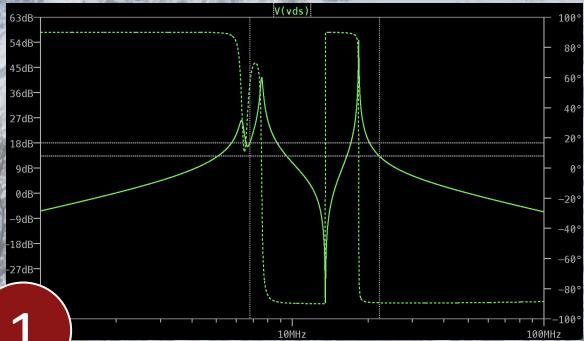

1
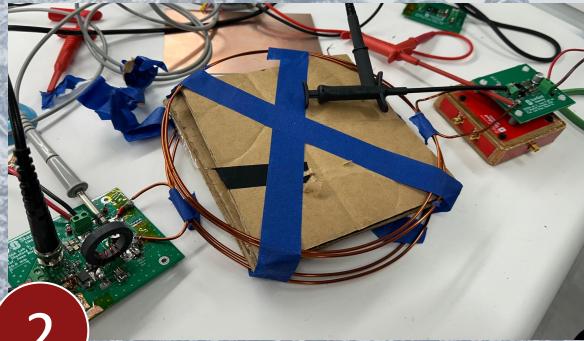
## Inverter Specification and Design


- Project Requirements
- Resonant converter Overview
- Design and Strategy



2
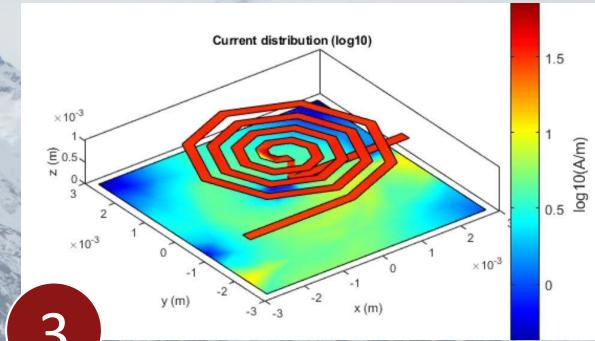
## Inverter Implementation, Testing, and Results

- Inverter
- Transformer Coil
- Testing and Results



3



## Manufacturing and Next Steps (lessons from De-Ice)

- Reviewing main manufacturing issues
- Manufacturing Magnetics

A large, semi-transparent watermark of the Stanford University logo is positioned on the left side of the slide, consisting of a grid of interlocking circular patterns.


# Thank You

# ZVS and ZCS

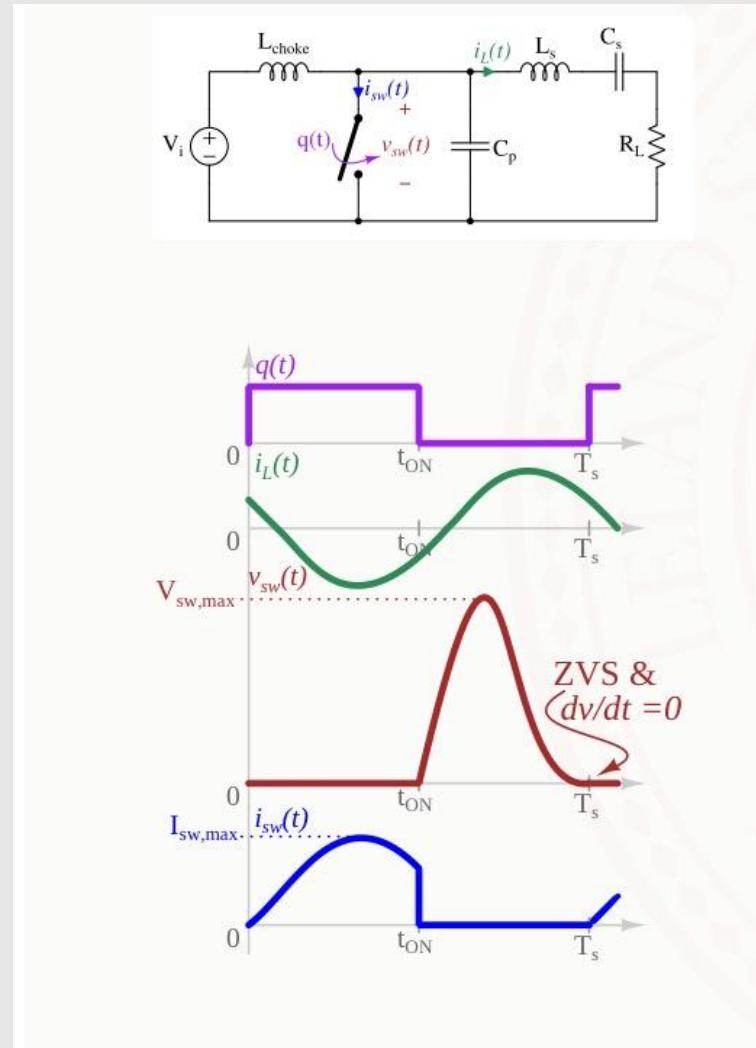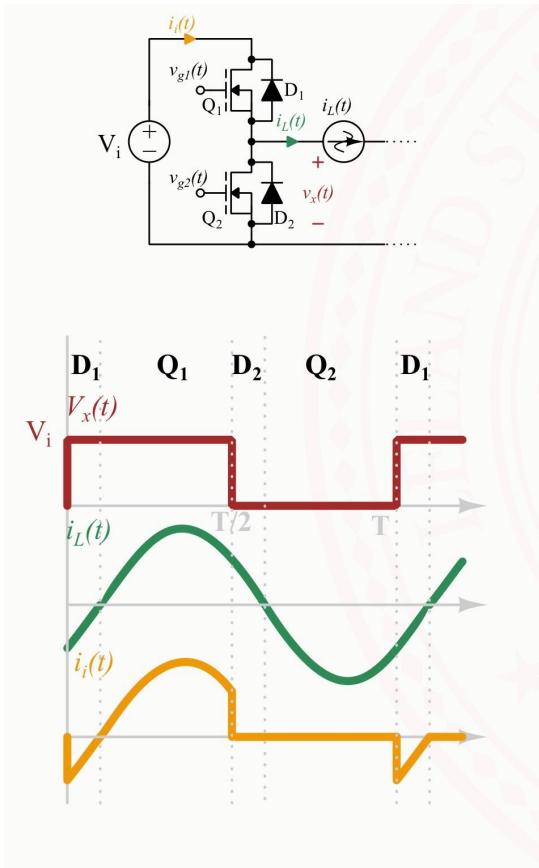

# Why operate at high frequencies?

## Small Components

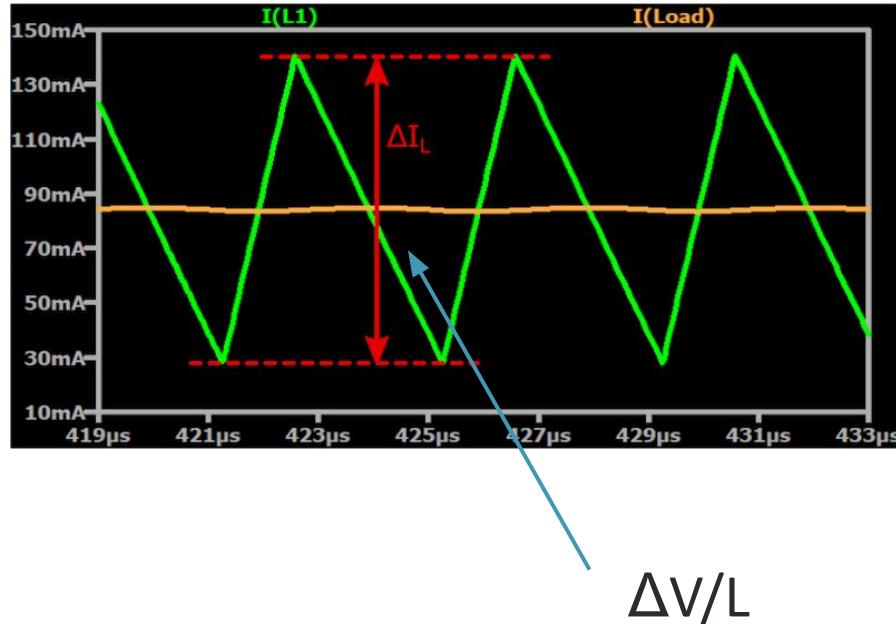

But Higher Switching Losses

## Energy loss in RC circuits

How much energy reaches the capacitor? How much energy is delivered by the source?

$$\begin{aligned} E_C &= \int_0^{\infty} v_C i_C dt \\ &= \int_{q(t=0)}^{q(t \rightarrow \infty)} v_C dq \\ &= \int_{v_C(t=0)}^{v_C(t \rightarrow \infty)} C v_C dv_C \\ E_C &= \frac{1}{2} C V_i^2 \end{aligned}$$

$$\begin{aligned} E_{source} &= \int_0^{\infty} V_i i_C dt \\ &= V_i \int_{q(t=0)}^{q(t \rightarrow \infty)} dq \\ &= C V_i \int_{v_C(t=0)}^{v_C(t \rightarrow \infty)} dv_C \\ E_{source} &= C V_i^2 \end{aligned}$$

# Resonant Topologies and filtering


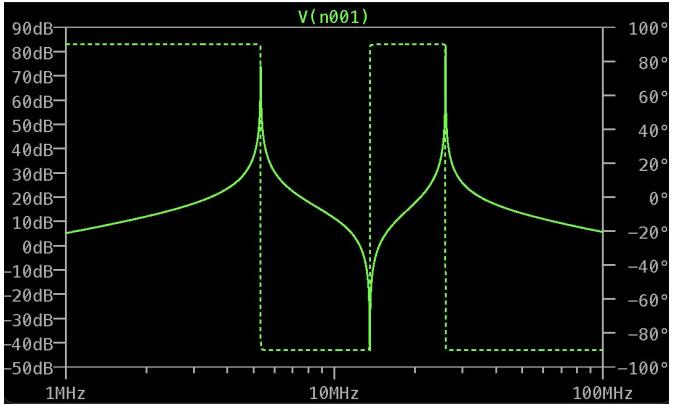
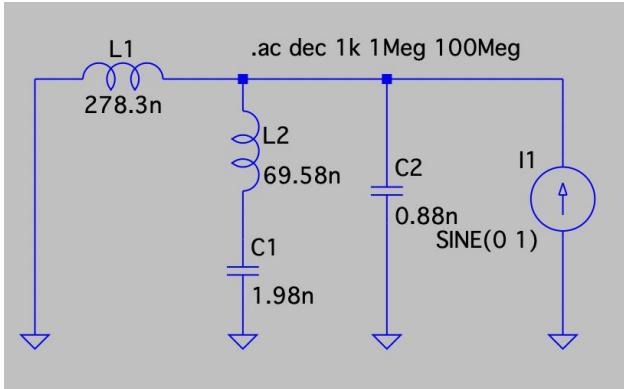



Fig. 19.34 Series, parallel, and LCC resonant tank networks, and their input impedances  $Z_{i0}$  and  $Z_{i\infty}$ .

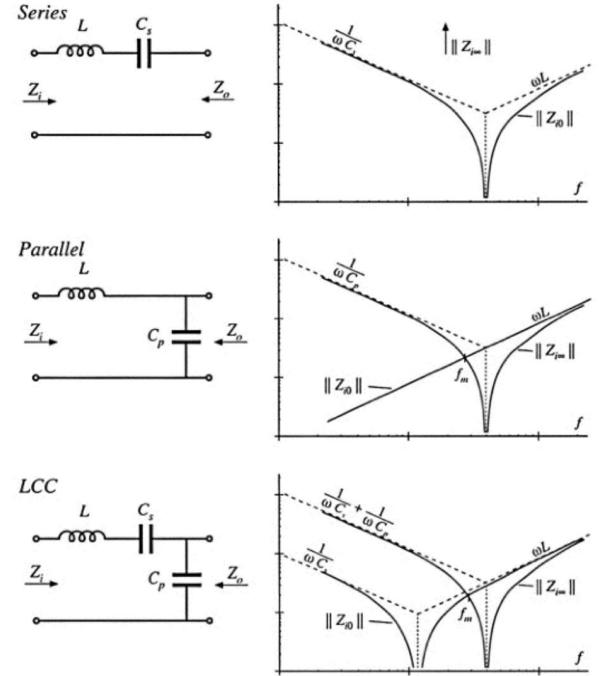19.4 Load-Dependent Properties of Resonant Converters 731




# Results Data


Pout Vs Rload

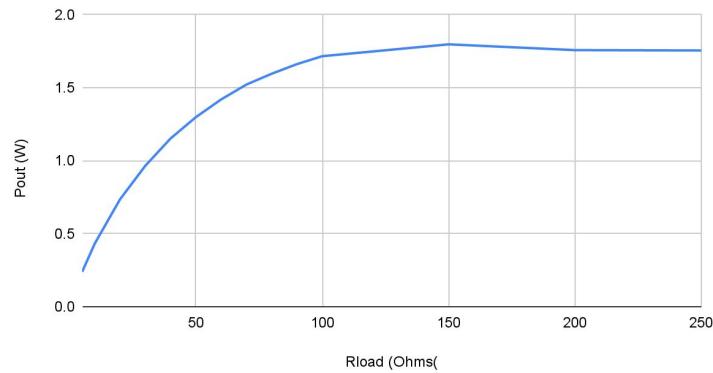


Efficiency Vs Vin

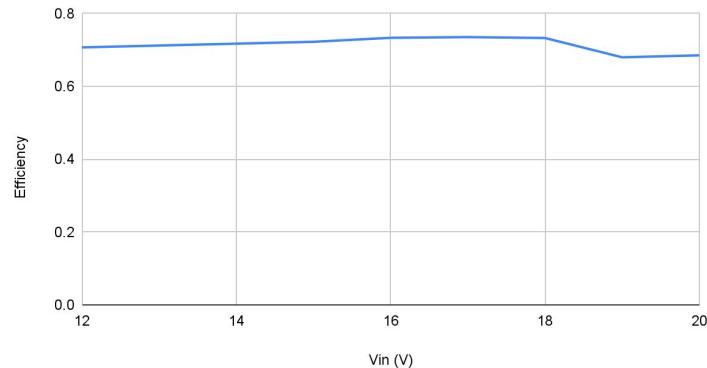

Pout Vs Fsw

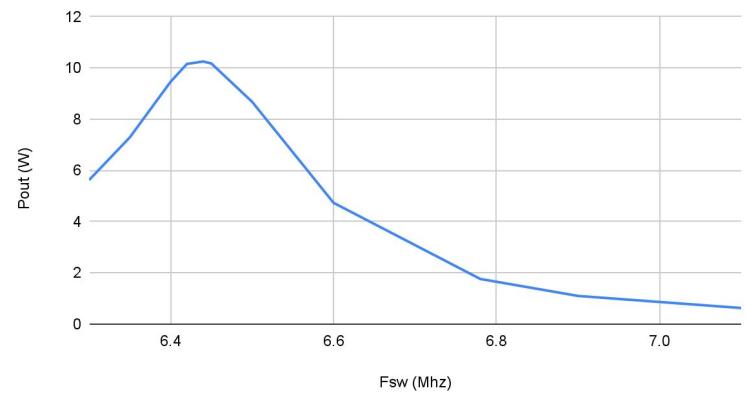

Pout Vs Vin

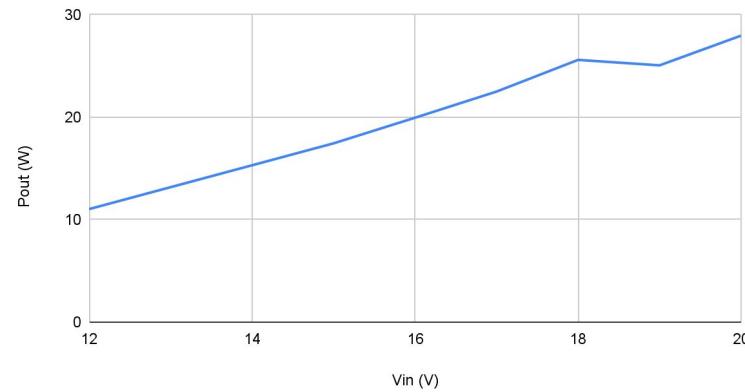

# Spiral Inductor Equations

$$L = K_1 \mu_0 \frac{N^2 D_{avg}}{1 + K_2 \varphi}$$

